



Bias Current Problem

1. What is the required Value of R_x to cancel the effect of I_b at the output?
2. If $I_b = 120\text{nA}$ and $R_x = 200\text{k}$, what is the Voltage error present at the output?